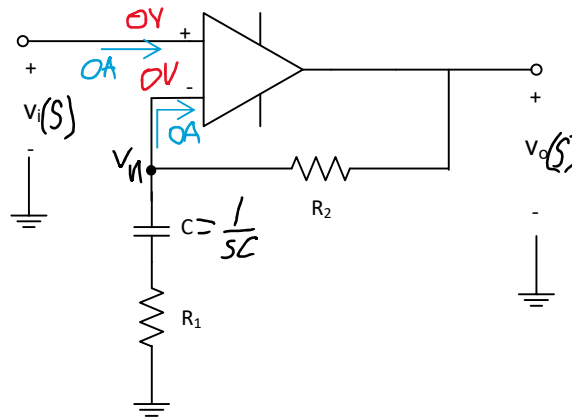


Active Filter Design and Verification

1. In the active circuit shown below the op amp can be considered ideal. Analyze the circuit to derive the expression for the transfer function $H(s)=V_o(s)/V_i(s)$.

$$v_n = v_i(s)$$



Verification that the transfer function is equal to the following (equation 1):

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{R_1 + R_2}{R_1} \frac{s + \frac{1}{(R_1 + R_2)C}}{s + \frac{1}{R_1 C}}$$

$$\frac{v_i(s) - v_o(s)}{R_2} + \frac{v_i(s) - 0}{\frac{1}{sC} + R_1} + 0 = 0$$

$$\frac{1}{R_2} v_i(s) - \frac{1}{R_2} v_o(s) = -\frac{v_i(s)}{\frac{1}{sC} + R_1}$$

$$\frac{1}{R_2} v_i(s) + \frac{1}{\frac{1}{sC} + R_1} v_i(s) = \frac{1}{R_2} v_o(s)$$

$$v_i(s) \left[\frac{1}{R_2} + \frac{1}{\frac{1}{sC} + R_1} \right] = \frac{1}{R_2} v_o(s)$$

$$R_2 \left[\frac{1}{R_2} + \frac{1}{\frac{1}{sC} + R_1} \right] = \frac{v_o(s)}{v_i(s)}$$

$$1 + \frac{R_2}{\frac{1}{sC} + R_1} = \frac{v_o(s)}{v_i(s)}$$

$$\frac{\frac{1}{sC} + R_1 + R_2}{\frac{1}{sC} + R_1} = \frac{v_o(s)}{v_i(s)}$$

$$\frac{\frac{1 + R_1 sC + R_2 sC}{sC}}{\frac{1 + R_1 sC}{sC}} = \frac{v_o(s)}{v_i(s)}$$

$$\begin{aligned}
\frac{1 + R_1 sC + R_2 sC}{1 + R_1 sC} &= \frac{v_o(s)}{v_i(s)} \\
\frac{1 + sC(R_1 + R_2)}{\left[s + \frac{1}{CR_1}\right] CR_1} &= \frac{v_o(s)}{v_i(s)} \\
\frac{C(R_1 + R_2)}{CR_1} * \frac{s + \frac{1}{(R_1 + R_2)C}}{s + \frac{1}{R_1 C}} &= \frac{v_o(s)}{v_i(s)} \\
\frac{R_1 + R_2}{R_1} \frac{s + \frac{1}{(R_1 + R_2)C}}{s + \frac{1}{R_1 C}} &= \frac{v_o(s)}{v_i(s)}
\end{aligned}$$

2. Choose numerical values for the resistors (in k Ω range) and the capacitor (in microfarad range). Choose $R_2 > R_1$. Substitute the values of the resistors and the capacitor in the equation above. Input the transfer function into MATLAB and generate its Bode plot.

let $R_2 = 2 \text{ k}\Omega$ & $R_1 = 1 \text{ k}\Omega$ & $C = 2 \text{ }\mu\text{F}$:

$$H(s) = \frac{1k + 2k}{1k} \frac{s + \frac{1}{(1k+2k)2\mu}}{s + \frac{1}{(1k)(2\mu)}} = 3000 \left[\frac{s + 166.67}{s + 0.002} \right] = \frac{3000s + 500000}{s + 0.002}$$

note:


$$H(s) = \frac{K}{s + 0.002}$$

$$K = (s + 0.002) * H(s) = 3000s + 500000|_{s=-0.002} = 499994$$

$$L^{-1}\{H(s)\} = h(t) = K e^{-at} u(t)$$

$$h(t) = 499994 e^{-0.002t} u(t)$$

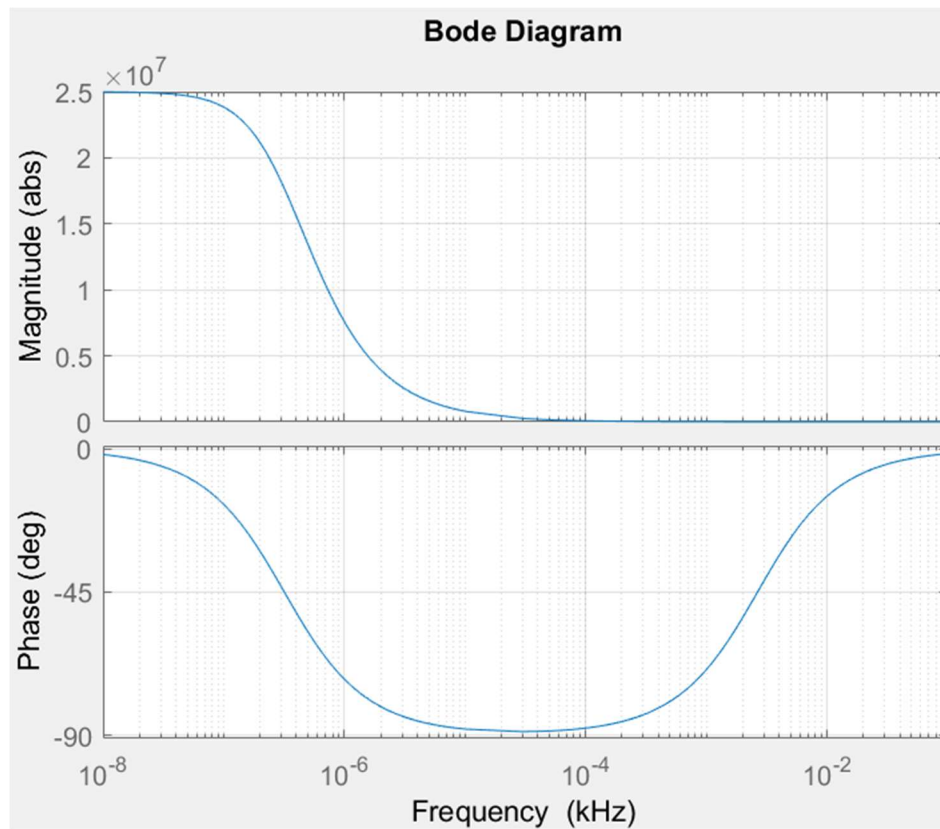Bode plot from MATLAB: plot is of a Low-pass filter



Command Window

```
>> n = [3000 50000];
>> d = [1 0.002];
>> h = tf(n,d)
Dot indexing is not supported for variables of this type.
```

```
>> h = tf(n,d)
```

h =

$$\frac{3000 s + 50000}{s + 0.002}$$

Continuous-time transfer function.

```
fx >> bode(h)
```

3. Substitute $s=j\omega$ in equation 1 above to obtain $H(j\omega)$. Find the magnitude function of $H(j\omega)$, $|H(j\omega)|$, in terms of R_1 , R_2 , C and ω . Evaluate $|H(j\omega)|$ at $\omega=0$ and at $\omega=\infty$. Verify that these results agree with the numerical results from MATLAB.

$$H(j\omega) = \frac{R_1 + R_2 \frac{1}{(R_1+R_2)C} + j\omega}{R_1 \frac{1}{R_1 C} + j\omega}$$

$$H(j\omega) = \frac{R_1 + R_2}{R_1} * \frac{1 + j\omega(R_1 + R_2)C}{(R_1 + R_2)C} * \frac{R_1 C}{1 + j\omega R_1 C} = \frac{1 + j\omega(R_1 + R_2)C}{1 + j\omega R_1 C}$$

$$|H(j\omega)| = \frac{\sqrt{1^2 + \omega^2(R_1 + R_2)^2 C^2}}{\sqrt{1^2 + \omega^2 R_1^2 C^2}} = \frac{\sqrt{1 + \omega^2(R_1 + R_2)^2 C^2}}{\sqrt{1 + \omega^2 R_1^2 C^2}}$$

$|H(j\omega)|$ @ $\omega = 0$:

$$|H(j0)| = \frac{\sqrt{1+0}}{\sqrt{1+0}} = 1$$

$|H(j\omega)|$ @ $\omega = \infty$:

$$|H(j\infty)| = \frac{(R_1 + R_2)}{R_1} \frac{\sqrt{\frac{1}{(R_1+R_2)^2 C^2} + \infty^2}}{\sqrt{\frac{1}{R_1^2 C^2} + \infty^2}}$$

$$|H(j\infty)| = \frac{(R_1 + R_2)}{R_1} \lim_{x \rightarrow \infty} \left[\frac{\sqrt{\frac{1}{(R_1+R_2)^2 C^2} + x^2}}{\sqrt{\frac{1}{R_1^2 C^2} + x^2}} \right] = \frac{(R_1 + R_2)}{R_1} * \left[\frac{\sqrt{\frac{1/(R_1+R_2)^2 C^2}{\infty^2} + 1}}{\sqrt{\frac{1/R_1^2 C^2}{\infty^2} + 1}} \right]$$

This term $\rightarrow 0$

$$|H(j\infty)| = \frac{(R_1 + R_2)}{R_1} \frac{\sqrt{0+1}}{\sqrt{0+1}} = \frac{(R_1 + R_2)}{R_1}$$

This term $\rightarrow 0$

4. The filter cutoff frequency is the frequency where the magnitude is equal to its maximum value divided by $\sqrt{2}$ (or 0.7071 $|H(j\omega)|_{\max}$). Show that for $R_2 > R_1$ the expression for the filter cutoff frequency ω_c is equal to the following:

$$\omega_c = \frac{1}{C} \sqrt{\frac{1}{R_1^2} - \frac{2}{2(R_1 + R_2)^2}}$$

$$\frac{|H(j\omega)|_{\max}}{\sqrt{2}} = \frac{\frac{(R_1 + R_2)}{R_1}}{\sqrt{2}} = \frac{\sqrt{1 + \omega^2(R_1 + R_2)^2 C^2}}{\sqrt{1 + \omega^2 R_1^2 C^2}}$$

$$(R_1 + R_2)^2 (1 + \omega_c^2 R_1^2 C^2) = 2R_1^2 (1 + \omega_c^2 (R_1 + R_2)^2 C^2)$$

$$(R_1 + R_2)^2 + (R_1 + R_2)^2 (R_1 + R_2)^2 (1 + \omega_c^2 R_1^2 C^2) = 2R_1^2 + 2R_1^2 \omega_c^2 (R_1 + R_2)^2 C^2$$

$$(R_1 + R_2)^2 R_1^2 \omega_c^2 C^2 = (R_1 + R_2)^2 - 2R_1^2$$

$$R_1^2 \omega_c^2 C^2 = 1 - \frac{2R_1^2}{(R_1 + R_2)^2}$$

$$\omega_c^2 = \frac{1}{R_1^2 C^2} \left[1 - \frac{2R_1^2}{(R_1 + R_2)^2} \right]$$

$$\omega_c^2 = \frac{1}{C^2} \left[\frac{1}{R_1^2} - \frac{2R_1^2}{R_1^2 (R_1 + R_2)^2} \right]$$

$$\omega_c = \frac{1}{C} \sqrt{\frac{1}{R_1^2} - \frac{2R_1^2}{R_1^2 (R_1 + R_2)^2}}$$

5. Design the filter circuit for a cutoff frequency of 2000 Hz and a gain of 10 (V_o/V_{in}) in its passband. This step involves choosing values for R_1 , R_2 and C to meet the given specifications.

$$\text{gain} = \frac{V_o}{V_i} = 10 = \frac{R_1 + R_2}{R_1} \quad ; \quad \text{let } R_1 = 1\text{k}\Omega$$

$$\omega_c = 2000(2\pi) = 12566.37 \frac{\text{rad}}{\text{s}} = \frac{1}{C} \sqrt{\frac{1}{R_1^2} - \frac{2}{2(R_1 + R_2)^2}}$$

$$10 = \frac{1\text{k} + R_2}{1\text{k}}$$


$$10\text{k} = 1\text{k} + R_2 \rightarrow R_2 = 9\text{k}\Omega$$

$$\omega_c = 4000\pi = \frac{1}{C} \sqrt{\frac{1}{1\text{k}^2} - \frac{2}{2(1\text{k} + 9\text{k})^2}} = \frac{1}{C} \sqrt{9.9 \times 10^{-7}}$$

$$C = \frac{9.9499 * 10^{-4}}{4000\pi} = 7.9179 * 10^{-8} \rightarrow C = 79.18 \text{ nF}$$

$$H(s) = \frac{10k}{1k} \frac{s + \frac{1}{10(79.18)}}{s + \frac{1}{1k(79.18n)}} = 10 \frac{s + 1262.97}{s + 12629.7} = \frac{10s + 12629.7}{s + 12629.7}$$

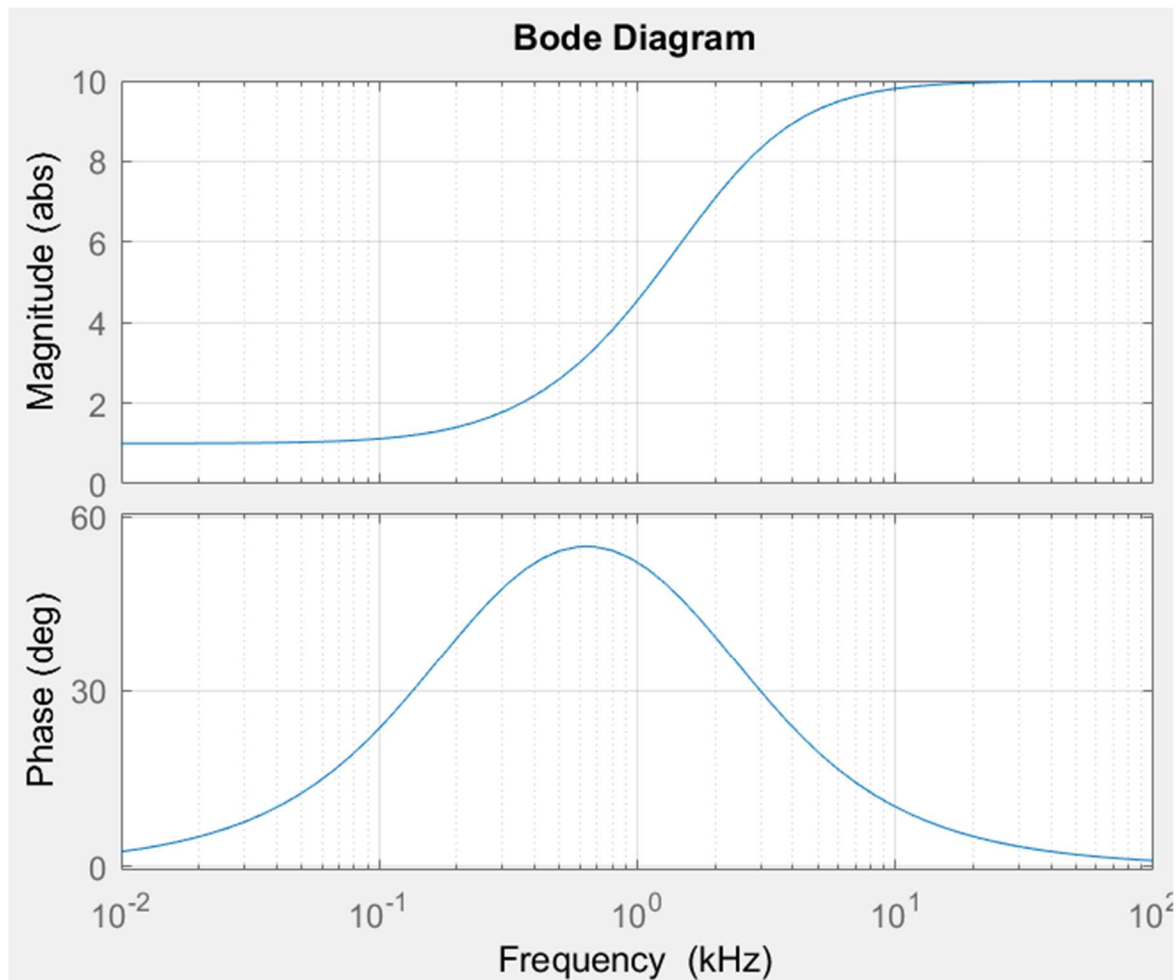6. Verify your filter design with MATLAB and LTspice. (Is a High-pass op amp filter)




```
>> clear
>> n = [10 12629.7];
>> d = [1 12629.7];
>> h = tf(n,d)

h =

    10 s + 1.263e04
    -----
         s + 1.263e04

Continuous-time transfer function.

>> bode(h)
fx >>
```

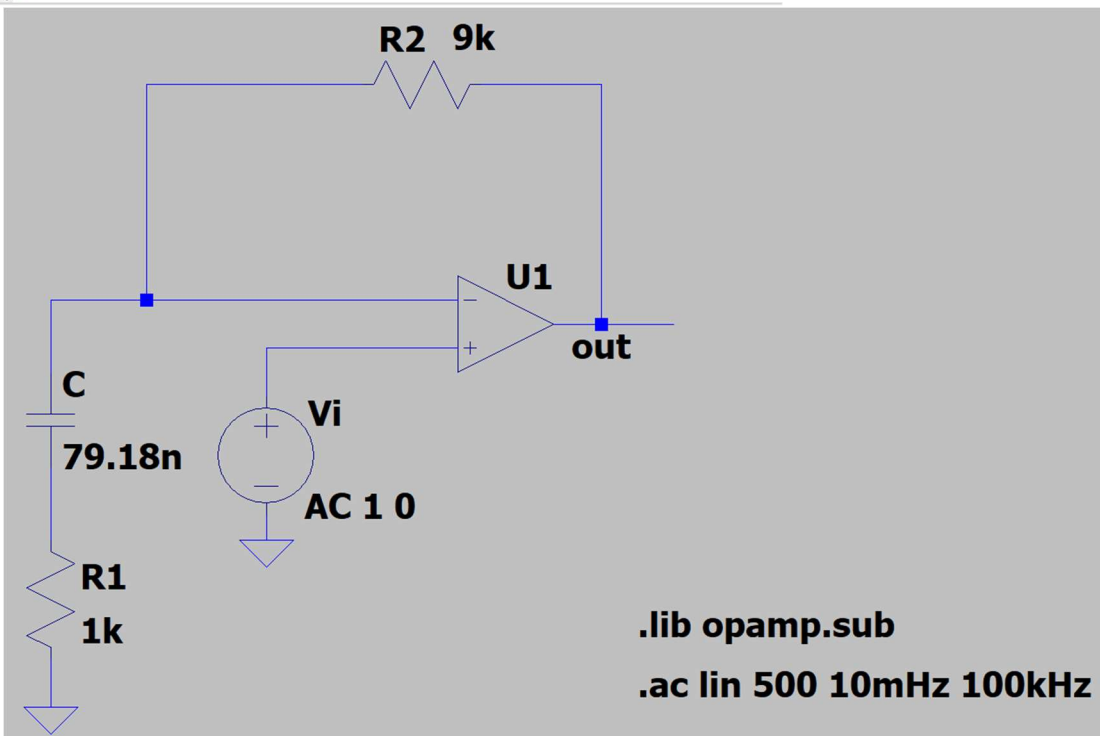

vertical axis is in volts and $V(n002) = V_i$ on schematic → so graph is of function: $V(\text{out})/V_i$

